

The current and voltage (I-V) curve of a photovoltaic cell. Maximum power produced

Scope: Record the current and voltage (*I-V*) curve of a photovoltaic (PV) cell. Determine the maximum power produced by the PV cell

Platform: Virtual tool. Resistive load, https://infinitypv.com/l/Potentiometer.php

The **Solar Cell** *I-V* **Characteristic Curve** gives a detailed description of its energy conversion efficiency. The maximum power produced P_m by a photovoltaic cell is a key parameter for PV applications design.



The virtual instrument *Resistive load, https://infinitypv.com/l/Potentiometer.php* allows the IV curve to be recorded for a PV cell using a potentiometer, a voltmeter, and an ammeter. If you have a smartphone, you can open the virtual instrument by scanning the QR barcode.



Remark: The virtual instrument is realized based on the circuit shown below:



Measure the voltage and current at different resistance of the load. With this information the power produced by the photovoltaic cell can be calculated as:

 $P = V \cdot I$

Use the virtual instrument by sliding the knob and record the highlighted values in the table below:

Resistance R [Ω]									
<i>V</i> [V]									
/ [A]									
<i>P</i> [W]									
V _{mp} [V]			<i>I_{mp}</i> [A]				<i>P</i> _m [W]		

Tips: - record as many values of the I-V pair for a more accurate graphical representation, **especially** *for high resistance values*.

- use MS Excel to record and graph the resulting data.

Graph the *I-V* and *P-V* curves and determine the values of: I_{mp} , V_{mp} and P_m .

Then, validate the correctness of your results using the equation:

 $P_m = V_{mp} \cdot I_{mp}$

Prepare a short presentation (a pptx file is recommended) about your experiment, results, interpretation, ... to be shared with all participants.

References

[1] <u>https://fr.mathworks.com/help/physmod/sps/powersys/ref/pvarray.html.</u>

[2] <u>https://infinitypv.com/learn/virtual-tools/c04</u>.